

Sub V_T

$$g_m = \frac{K I_{bias}}{V_T}$$

$$r_o = \frac{V_A}{I_{bias}}$$

$$a_v = -g_m r_o = -\frac{K V_A}{V_T}$$

Above V_T

$$g_m = \sqrt{2K I_{bias}}$$

$$r_o = \frac{V_A}{I_{bias}}$$

$$a_v = -g_m r_o = -\frac{V_A \sqrt{2K}}{\sqrt{I_{bias}}}$$

for $W = 7 \mu m$ $L = 2 \mu m$	$I_D = 100 nA$ $V_A = 2.89 V$	$I_D = 100 \mu A$ $V_A = 69.1 V$
------------------------------------	----------------------------------	-------------------------------------

Now for $I_D = 100 nA, V_A = 2.89 V$

Sub $r_o = \frac{2.89 V}{100 nA} = 28.9 M\Omega$

above $r_o = \frac{69.1 V}{100 \mu A} = 69.1 \mu\Omega$

$$I_D = \frac{1}{2} K (V_{gs} - V_T)^2 \left(1 + \frac{V_{ds}}{V_A}\right)$$

To determine V_T lots do a Test
simulation of $1 f_0 t$ with $W = 7 \mu m, L = 2 \mu m$

Sweep the V_g and then Plot $g_{m+}(I_D)$

Next get the slope of the Linear Region

which is 0.0127

$$V_{Th} = V_{GS} - \frac{I_D}{\text{slope}}$$

Say $V_{Th} = (1.00) - \frac{0.00768}{0.0127} = 0.398V$

Now on Test sim when $V_g = 0.398$

then we get $I_{Th} \approx 44.59 \text{ nA}$

Therefore the above Sub and Above bias currents are wrong.

So we pick $W = 7\mu\text{m}$ and $L = 2\mu\text{m}$


Now we need to find I_{bias}

$$So \text{ } a_v = -50, -300$$

$$I_D = \frac{1}{2} K (V_{GS} - V_T)^2 \left(1 + \frac{V_{DS}}{V_A}\right)$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \left(1 + \frac{V_{DS}}{V_A}\right)$$

From Square Law Plot

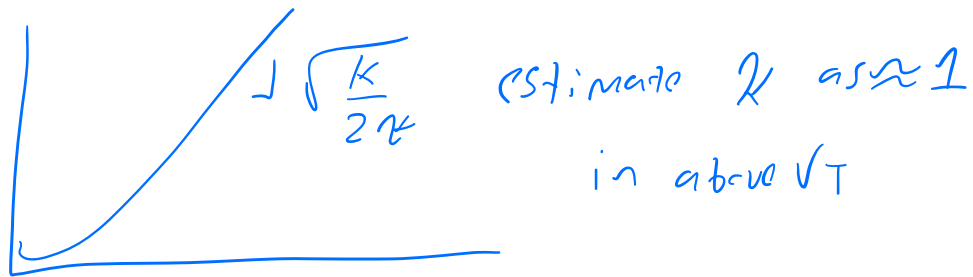

$$\text{new } \sqrt{\frac{1}{2} k} = \text{slope}$$

$$= \sqrt{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} = S$$

$$S^2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$$

$$\mu_n C_{ox} = \frac{2S^2}{\frac{W}{L}}$$

$$\text{slope} \approx 0.0125 \frac{\sqrt{A}}{V}$$

$$\mu_n C_{ox} = \frac{2(0.0125)^2 A}{\frac{W}{L}}$$

$$\mu_n C_{ox} = 4.464 \times 10^{-5}$$

List of Parameters

$$k' = 44.6 \frac{\mu A}{V^2}$$

$$V_{th} = 0.398 V$$

$$I_{th} = 44.59 \mu A$$

$$W = 7 \mu m$$

$$L = 2 \mu m$$

$$a_v = -50, -3 \text{ } \omega$$

$$above \quad V_T = 7 \quad g_m = \sqrt{2k'I}$$

Lets use the graph of

$$\frac{d(I_D)}{d(V_{GS})}$$

to determine g_m at
the amplification region (0 to 1V) ^{or from graphs}

$$0-0.9 \text{ avg } g_m = 185.9 \mu S$$

~~now use that to find r_o for gain of -300~~

$$-a_v = -g_m r_o$$

$$r_o = \frac{300}{185.9 \mu S} = 1613770 = 1.6 M\Omega$$

Now we have

List of Parameters

$$k' = 44.6 \frac{\mu A}{V^2}$$

$$V_{th} = 0.398 V$$

$$I_{th} = 44.59 \mu A$$

$$W = 7 \mu m$$

$$L = 2 \mu m$$

$$a_v = -50, -300$$

$$g_m \propto 185.9 \mu S$$

$$r_o \propto 1.6 M\Omega$$

~~Find I_{bias}~~

$$g_m = \sqrt{2k' \frac{W}{L} I_D}$$

$$I_D = \frac{(g_m)^2}{2k' \frac{W}{L}} = \frac{(188.9 \mu S)^2}{2(41.6 \frac{\mu A}{V^2})(\frac{7}{2})}$$

$$I_D = 110 \mu A$$

for above V_t gain ≈ -50

New for $a_v = -300$

List of Parameters

$$k' = 44.6 \frac{\mu A}{V^2}$$

$$V_{th} = 0.398 V$$

$$I_{th} = 44.59 \mu A$$

$$W = 7 \mu m$$

$$L = 2 \mu m$$

$$a_v = -50, -3 \text{ CO}$$

$$g_m = \sqrt{2k'I_{G:ns}}$$

$$r_o = \frac{V_A}{I_{G:ns}}$$

$$a_v = -g_m r_o$$

$$-a_v = \frac{V_A \sqrt{2 \cdot \frac{1}{2} k' \frac{W}{L} I_D}}{I_D}$$

avg V_A for above V_T for $k_{STH} 2$

$$= 27.55 V$$

$$S_o - S_o = \frac{(27.55)(\sqrt{44.9 \mu \cdot \frac{2}{3} \cdot I_D})}{I_D}$$

$$-S_o I_D = 27.55 \sqrt{1.5715 \times 10^{-4} I_D}$$

$$-1.8148 I_D = \sqrt{1.5715 \times 10^{-4} I_D}$$

$$3.294 I_D^2 = 1.5715 \times 10^{-4} I_D$$

$$I_D \approx 48 \mu A$$

a ballpark number

Guess and check around there

New Gain of ~ 300 Lets use subthreshold
for a higher gain

$$g_m = \frac{K I_{bias}}{V_T}$$

$$r_o = \frac{V_A}{I_{bias}}$$

$$-300 = \frac{(2.89) \sqrt{1.5715 \times 10^{-4} I_D}}{I_D}$$

$$(30.334 I_D)^2 = 1.5715 \times 10^{-4} I_D$$

$$a_v = -g_m r_o = -\frac{\mu V_A}{V_T}$$

$$g_{m0.1} I_D = 1.5715 \times 10^{-4}$$

$$I_D = 164 \text{ nA}$$

doing drains waves show that

$$\frac{W}{L} = \frac{7}{5} \text{ never reaches } -300 \text{ for gain}$$

$$\text{Switching } \frac{W}{L} = \frac{7}{4} \text{ Sweeps show reaches}$$

$$a_v = 300 \text{ around } 0.1 \rightarrow 10 \text{ nA range,}$$

So fine tune with one sweep
for $\approx 1 \text{ nA}$